Lab 5 - Modulo-n Counters

Brennan Pinette A01073920


March 2, 2021

Code:


/*

```
Brennan Pinette
   A01073920
  March 2, 2020
   This code will incremented count up if ONLY up is asserted, decrement count down
   if ONLY down is asserted. Count will be set to 0 if up and down are BOTH asserted.
   If neither are asserted count will not change.
*/
module modncount
                                      // up/down controls, cloc,
       input logic up, down, clock,
                                        // modulo-n count value
       output logic [3:0] count,
       output logic carry, borrow
                                         // carry/borrow
       );
       // my solution is here
       logic [3:0] count_next;
       assign carry =
           (count == 4'd4 && up )&& !down ? '1 :
           (count == '0 && !up )&& down ? '0:
           up && down ? '1 : '0 ;
       assign borrow =
           (count == 4'd4 && up) && !down ? '0 :
           (count == '0 && !up) && down ? '1:
           up && down ? '1 : '0 ;
       always_ff@(posedge clock) count = count_next ;
       assign count_next =
           !up && !down ? count :
           up && !down ? (count == 4'd4 ? 4'b0000 : count + 1'b1 ) :
           down && !up ? (count == 4'b0000 ? 4'd4 : count - 1'b1 ) :
           '0;
```

Block Diagram:

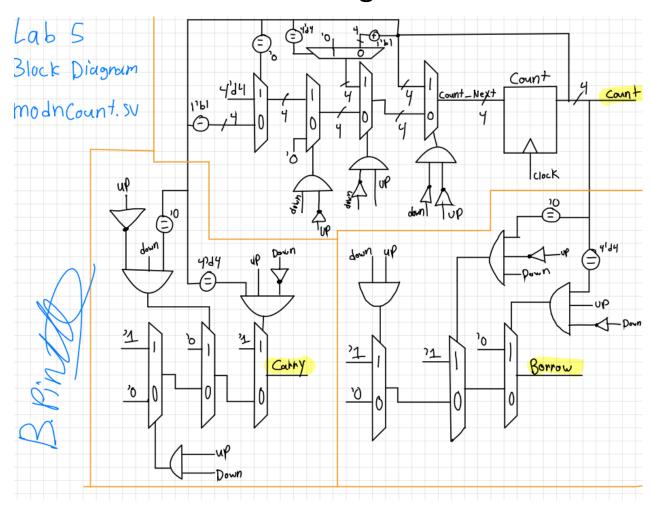

Compilation Report:

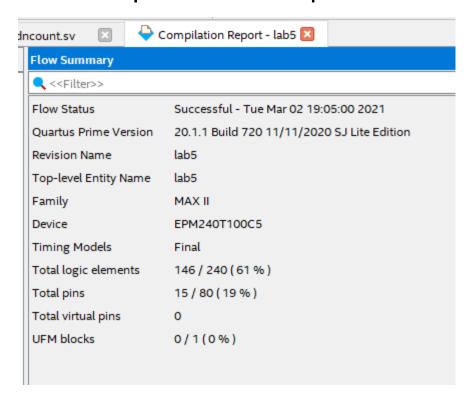

RTL:

